

PSU Clamp Test Waveforms & Calculations

April & May 2025

Table of Contents

Setup.....	1
Method.....	1
Supply rail voltages & mosfet gate voltage.....	2
currents.....	3
Mosfet Safe Operating Area (SOA) & Thermal considerations.....	6

Setup

Motor: EMAX ECO 1106, $K_v = 6000$, 12 magnets, with flywheel

Connections: Separate connection from power supply to Remora & from power supply to the clamp circuit

Clamp Circuit Schematic 	<p>Q1: the prototype used SQJ140ELP mounted on a copper sheet 15mm × 8mm × 0.5mm</p> <p>A few other possible mosfet candidates:</p> <table><thead><tr><th>Part Number</th><th>Package</th></tr></thead><tbody><tr><td>SQJ140ELP</td><td>PowerPAK (5x6)</td></tr><tr><td>SQJ160EP</td><td>PowerPAK (5x6)</td></tr><tr><td>IRFS7437</td><td>D²PAK</td></tr><tr><td>SQM40016EM</td><td>D²PAK 7 lead</td></tr><tr><td>RFP50N06</td><td>TO-220</td></tr><tr><td>SUP50020EL</td><td>TO-220</td></tr><tr><td>IRLB3034</td><td>TO-220</td></tr></tbody></table> <p>Q2: the prototype used KSA733, but almost any small PNP transistor would work.</p>	Part Number	Package	SQJ140ELP	PowerPAK (5x6)	SQJ160EP	PowerPAK (5x6)	IRFS7437	D ² PAK	SQM40016EM	D ² PAK 7 lead	RFP50N06	TO-220	SUP50020EL	TO-220	IRLB3034	TO-220
Part Number	Package																
SQJ140ELP	PowerPAK (5x6)																
SQJ160EP	PowerPAK (5x6)																
IRFS7437	D ² PAK																
SQM40016EM	D ² PAK 7 lead																
RFP50N06	TO-220																
SUP50020EL	TO-220																
IRLB3034	TO-220																

Method

In the ESC32 menu move slider right then left, this rapidly stops the motor sending energy back to the power supply (PSU), as power supplies only source current this raises the PSU voltage. The clamp is designed to start operating at about 12.5V preventing damage to the WiFi and Remora.

```
ESCAPE32 rev11 [MA_1]
Temp: 19C
Volt: 0.00V
Curr: 0.00A
Csum: 0mAh
ERPM: 186335
```



(slide right and left to arm)


$ERPM = rpm \times \text{pole pairs} \quad \therefore rpm = ERPM \div \text{pole pairs} \quad \therefore rpm = 186335 \div 6 = 31056rpm$

From K_v value: $rpm \approx 5V \times 6000K_v = 30000rpm$, so in reasonable agreement with ERPM reading from ESC32.

Commutation frequency, $F_c = (rpm / 60) \times \text{pole pairs} = ERPM / 60 = 186335 / 60 = 3106Hz$

Measured F_c from oscilloscope is 3003Hz

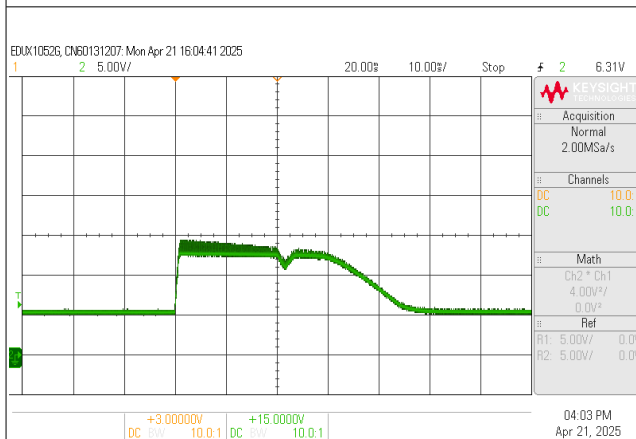Supply rail voltages & mosfet gate voltage




1

5V supply

green = supply at Remora, 5V/div, 10ms/div

Supply starts at 5V, then when the slider is moved left it rapidly rises to the clamp level of about 12.5V.

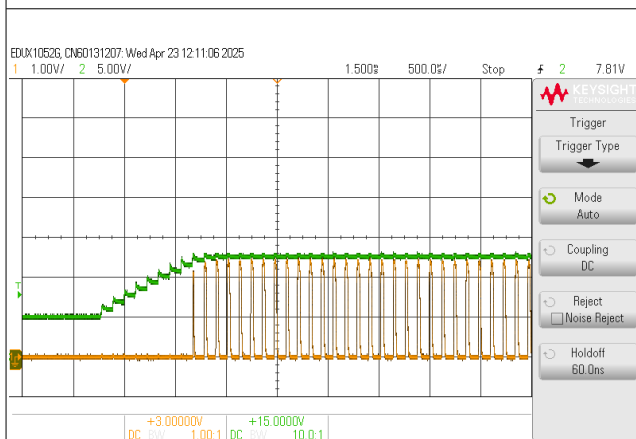The clamp successfully holds the voltage at below 15V.



2

5V supply


yellow = mosfet gate, 1V/div, 500μs/div

green = supply at clamp, 5V/div, 500μs/div

The pulses occur at 3× the commutation frequency. Initially at ≈115μs period ≈ 9kHz

Therefore one pulse for each of the ecom 3 phases.

See waveform 4 for an individual phase.

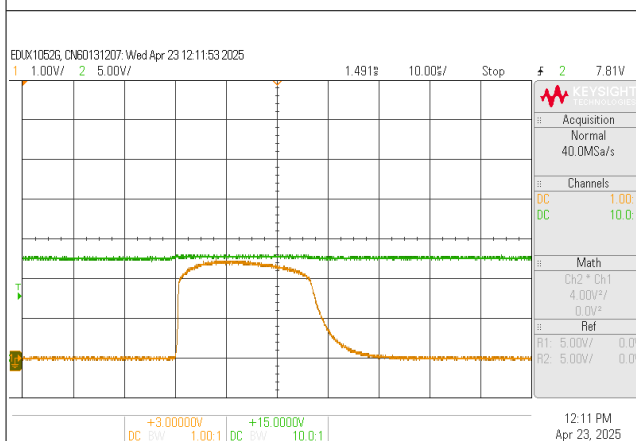

3, zoom of 2


5V supply

yellow = mosfet gate, 1V/div, 10μs/div

green = supply at clamp, 5V/div, 10μs/div

Gate voltage returning to zero indicates that the mosfet is being turned on & off during the clamping phase.

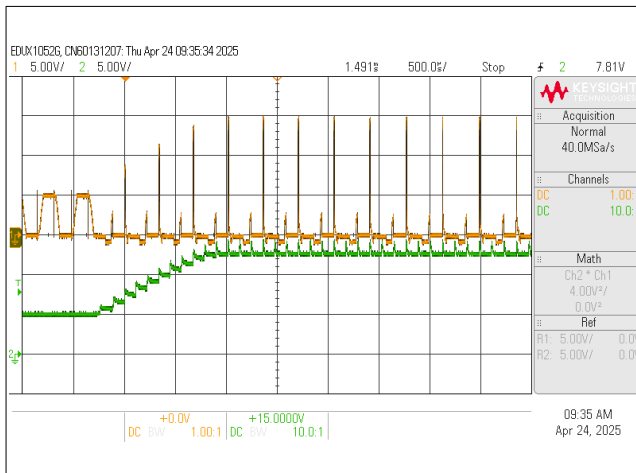The voltage remaining high must then be due to the capacitance in the PSU & Remora.




4
5V supply
yellow = ecom V phase output, 5V/div, 500μs/div
green = supply at Remora, 5V/div, 500μs/div

The high amplitude (>10V) spikes on V-phase occur at the commutation frequency.


currents

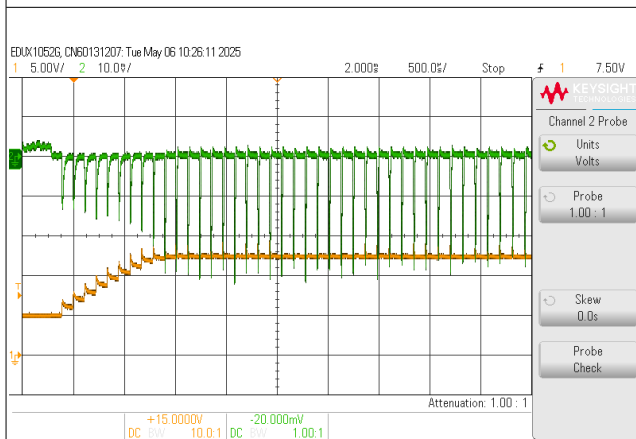(Remora settings slightly different to those for voltage measurements above, running at slightly higher rpm)



5
5V supply
yellow = supply at Remora, 5V/div, 500μs/div
green = current in Remora +ve line, 2A/div, 500μs/div

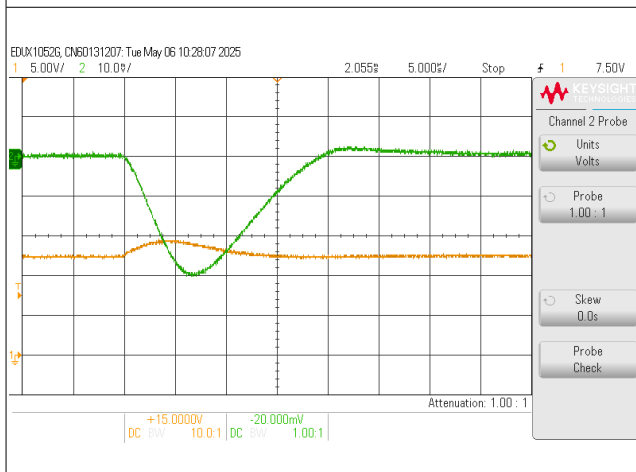
The spikes occur at 3× the commutation frequency, i.e. one for each phase.
Initially at ~ 110μs period




6 zoom of 5
5V supply
yellow = supply at Remora, 5V/div, 5μs/div
green = current in Remora +ve line, 2A/div, 5μs/div

6A peak current fed from Remora to PSU & clamp circuit.
Approximately a triangular shape width 20μs
So average current $\approx 6A \div 2 \times 40\mu s \div 110\mu s = 1.1A$

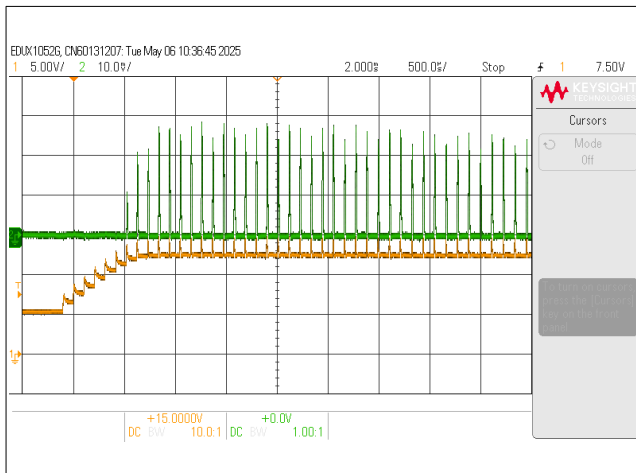The current & voltage both start to rise at the same time, but peak current is lags the peak PSU voltage by about 6.8μs



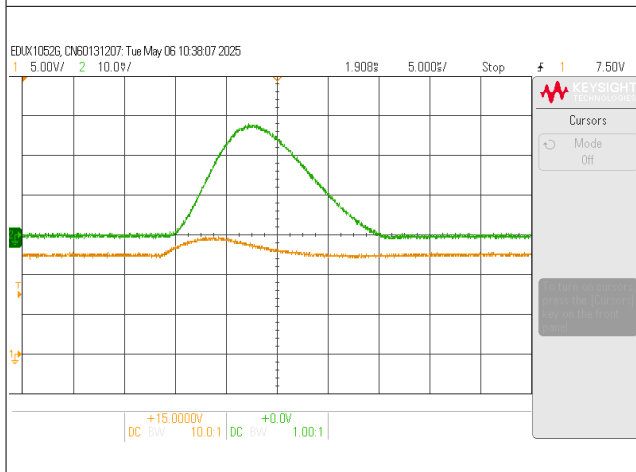
7
5V supply
yellow = supply at Remora, 5V/div, 500μs/div
green = current in clamp +ve line, 2A/div, 500μs/div




8 zoom of 7
5V supply
yellow = supply at Remora, 5V/div, 10μs/div
green = current in clamp +ve line, 2A/div, 10μs/div

peak current & width are very similar to the current from Remora, but some current must be flowing into the power supply output capacitor as indicated by the rise in the voltage.

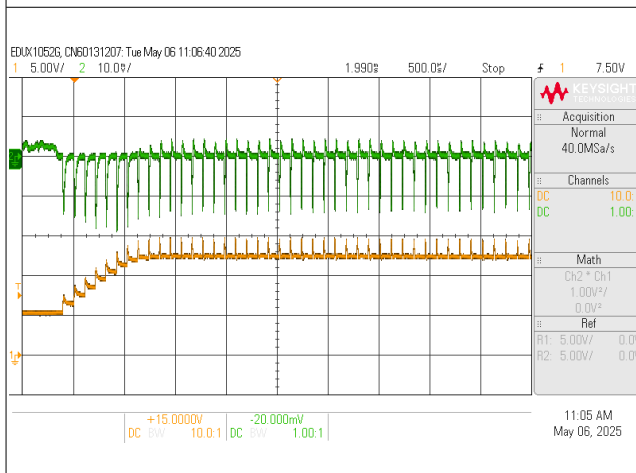The rise in current is delayed from the start of the voltage rise & the peak current lags the peak PSU voltage by about 9μs



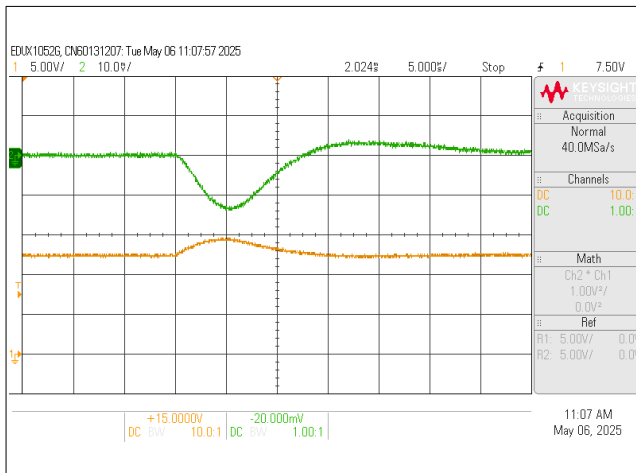9
5V supply
yellow = supply at Remora, 5V/div, 500μs/div
green = current in PSU +ve line, 2A/div, 500μs/div




10 zoom of 9

5V supply

yellow = supply at Remora, 5V/div, 5µs/div
green = current in PSU +ve line, 2A/div, 5µs/div

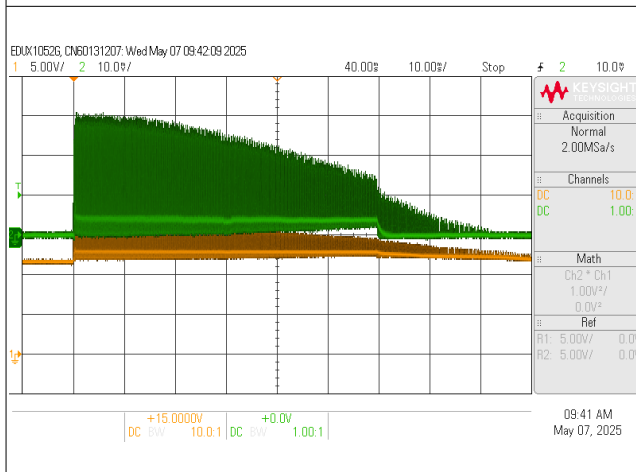
The current & voltage both start to rise at the same time, and peak current is coincident with the peak PSU voltage



11

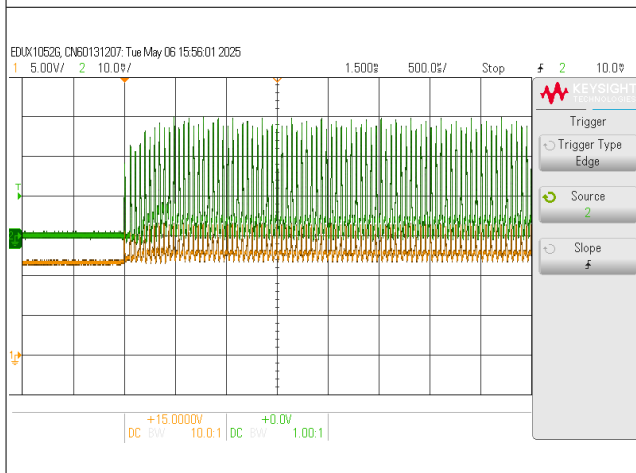11.5V supply


yellow = supply at Remora, 5V/div, 10ms/div
green = current in clamp +ve line, 5A/div, 10ms/div



12, as 11 but faster time-base

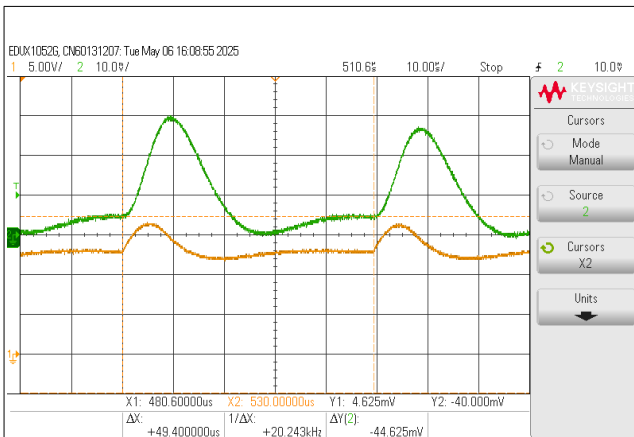11.5V supply

yellow = supply at Remora, 5V/div, 500µs/div
green = current in clamp +ve line, 5A/div, 500µs/div



Thermal calculations

just to get an estimate of whether a heatsink is required or not.

thermal energy formula: $Q = m \times c \times \Delta t$

Q = energy J

m = mass kg

c = specific heat capacity J / kg · K

Δt = temperature rise K (or °C)

If the energy was dumped in an aluminium heatsink

specific heat capacity = 900 J / kg · K

allow 20K temperature rise for the aluminium

∴ mass = 0.19g

If the energy was dumped in a copper sheet

specific heat capacity = 385 J / kg · K

allow 20K temperature rise for the copper sheet

∴ mass = 0.44g

For reference the total mass of a TO-220 is about 1.9g, so it may be able to absorb the energy without an additional heatsink.

Thermal simulation model

Using IRLB3034 in a TO-220 package as an example. Because it has a thermal model on the data-sheet. (Although it only has a moderate DC SOA its pulse SOA is acceptable).


Triangular power pulses applied with 55W average, see waveform 13.

R5 with a thermal resistance of 62K/W represents a TO-220 without a heatsink.


In the model:

current represents thermal power

voltage represents temperature

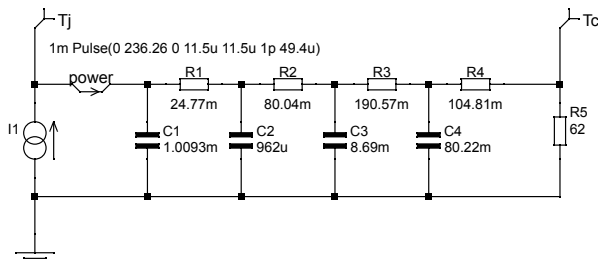

IRLB3034 thermal model results

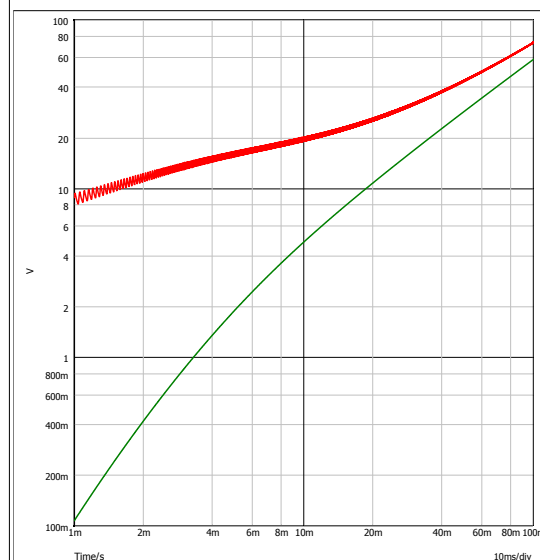

Red = junction temperature rise at 60ms, average = 50°C & temperature ripple due to the individual triangular power pulse is small at about 2°C.

green = TO-220 case temperature rise, at 60ms = 35°C

So a TO-220 package without a heatsink has an acceptable temperature rise for a single 60ms burst of pulses, even with an 11.5V supply.